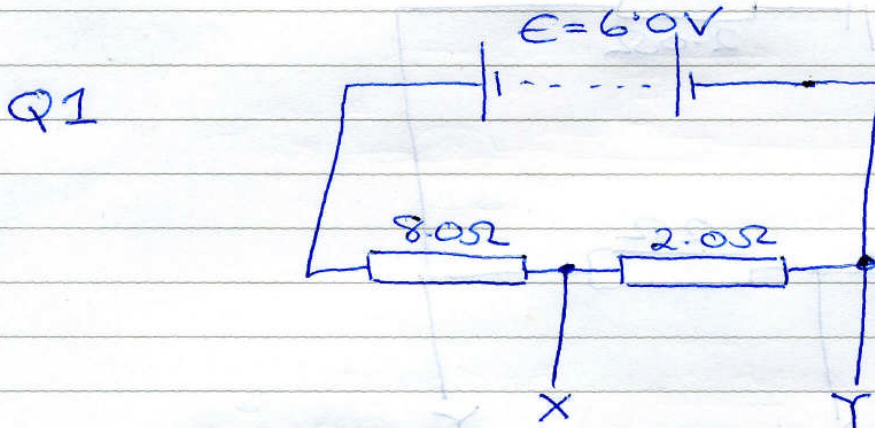


Low and Rounce - Exercise 20.8



By inspection

6.0V is shared by 10Ω
 \therefore each Ω gets 0.6V
 \therefore between X and Y the
pd is 1.2V

By calculation:-

$$E = I(R+r)$$

$$6.0 = I \times 10$$

$$\therefore I = 0.6 \text{ A}$$


$$E = 6.0 \text{ V}$$

$$r = 0 \Omega$$

$$R_{\text{TOT}} = 10 \Omega$$

\therefore over 2.0Ω resistor

$$2.0 \text{ V} = IR = 0.6 \times 2 = 1.2 \text{ V} \text{ Ans}$$

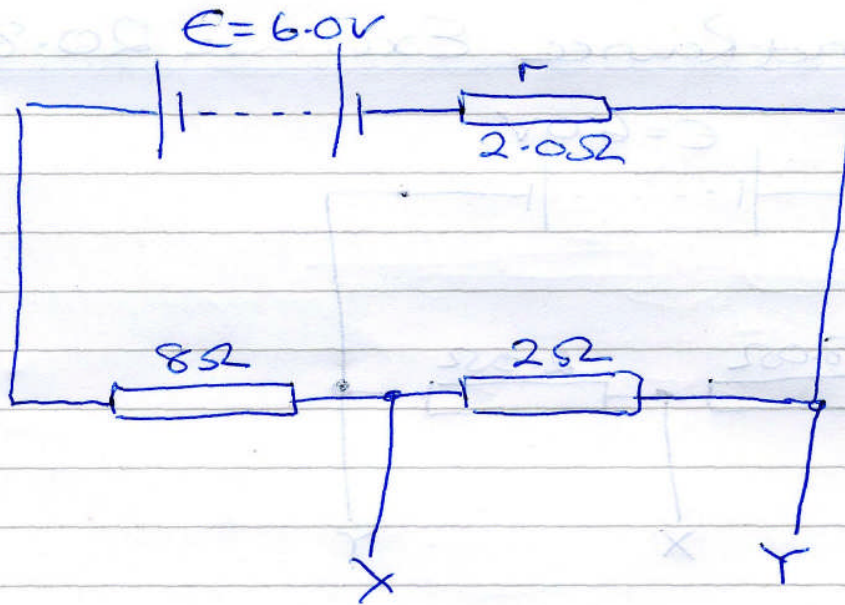

Now 6.0V is shared by 12Ω
 \therefore each Ω gets 0.5V and the
 pd between X and Y = 1.0V

$$E = I(R + r)$$

$$6.0 = I(10 + 2)$$

$$I = 0.5 \text{ A}$$

$$r = 2.0 \Omega$$

$$R = 10 \Omega$$

$$E = 6.0 \text{ V}$$


$$0.5 \times I = 0.5$$

$$A \times 0.5 = I$$

\therefore across 2Ω resistor

$$V = IR = 0.5 \times 2.0 = 1.0 \text{ V} \text{ Ans}$$

Q2.
(a)

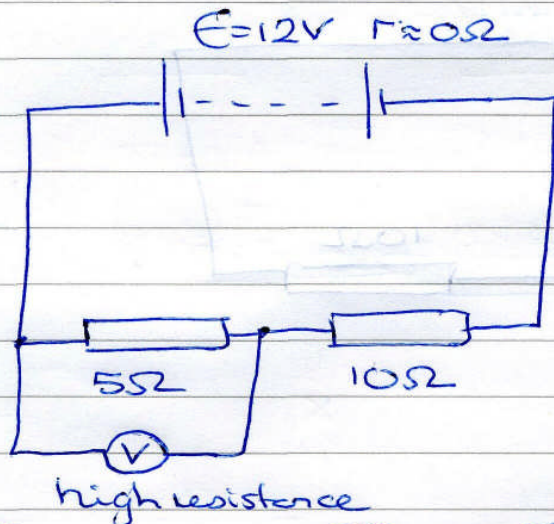

High resistance voltmeter - lets assume its resistance is ∞
Then, when we look at the combined resistance of 5Ω and the voltmeter

$$\frac{1}{R_{TOT}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{5} + \frac{1}{\infty} = \frac{1}{5} + 0$$

$$\therefore R_{TOT} = 5\Omega$$

~ this means adding a v. high resistance voltmeter does not interfere with the voltage distribution in the circuit.

By inspection — 4.0V

By calculation

$$E = I(R+r)$$

$$12 = I \times 15$$

$$\therefore I = 0.8A$$

$$V = IR$$

$$= 0.8 \times 5$$

$$= 4.0V$$



$$E = 12V$$

$$R_{TOT} = 15\Omega$$

$$r = 0\Omega$$

(b)

$$E = 12V, r = 0\Omega$$

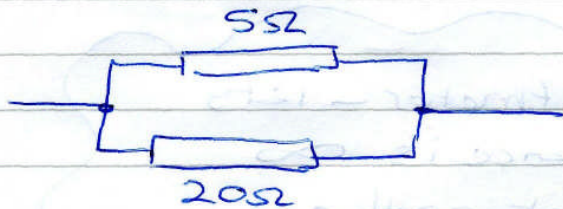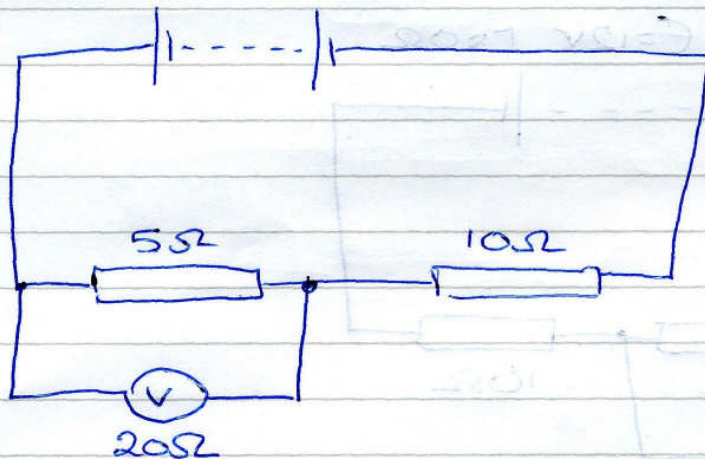


$$\frac{1}{R_{TOT}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{TOT}} = \frac{1}{5} + \frac{1}{20}$$

$$\frac{1}{R_{TOT}} = \frac{25}{100}$$


$$R_{TOT} = 4\Omega$$

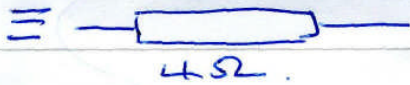

By Inspection - 14Ω share 12V

$\therefore 1\Omega$ gets $12/14$ and 4Ω gets $48/14$
 $= 3.4V$

By calculation

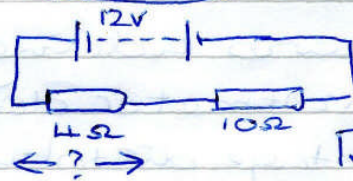

$$E = I(R + r)$$

$$12 = I(14 + 0)$$

$$I = 12/14 \text{ A}$$

$$R = 4 + 10 = 14\Omega$$

$$r = 0\Omega$$

$$E = 12V$$

$$V = IR = \frac{12}{14} \times 4 = 3.4V$$